Template Week 2 – Logic

Student number:564604

Assignment 2.1: Parking lot

Which gates do you need?

An AND gate is needed only

Complete this table

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Assignment 2.2: Android/iPhone

Which gates do you need?

The gate needed is exclusive OR (XOR)

Complete this table

Android phone	iPhone	Result (Phone in possession)
0	0	0
0	1	1
1	0	1
1	1	0

Assignment 2.3: Four NAND gates

Complete this table


Α	В	Q
0	0	0
0	1	0
1	0	0
1	1	1

How can the design be simplified?

The design can be simplified by directly using a single AND gate instead of four NAND gates, as the final output represents A. B this reduces how complexity and saves time


Assignment 2.4: Getting to know Logisim evolution

Screenshot of the design with your name and student number in it:

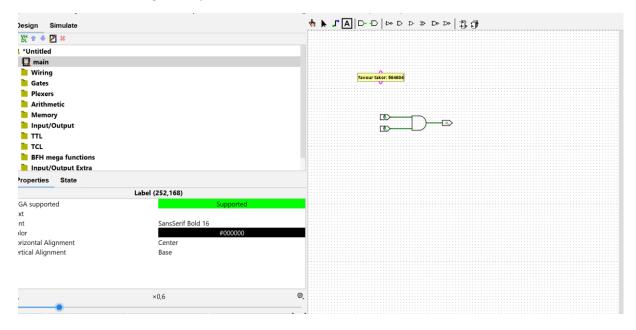


Assignment 2.5: SR Latch

Screenshot SR Latch in Logisim with your name and student number:

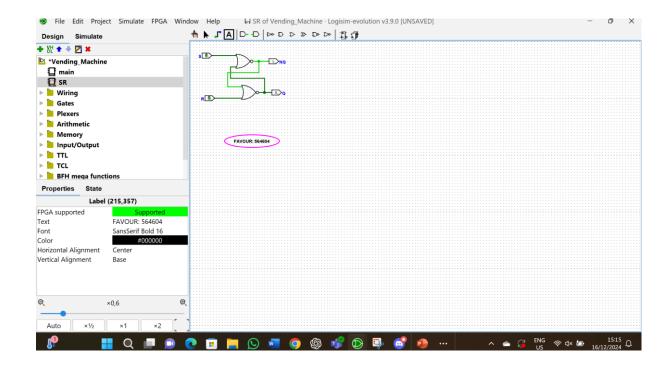

Assignment 2.6: Vending Machine

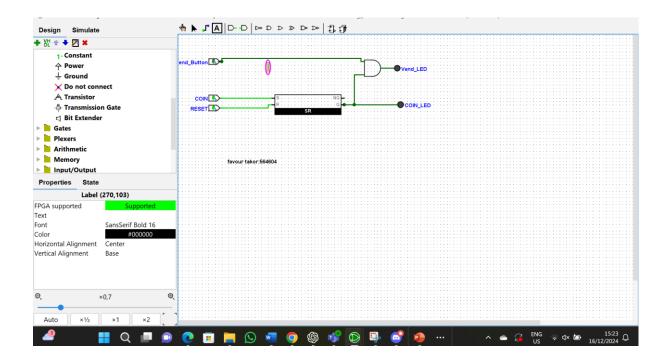Screenshot Vending Machine in Logisim with your name and student number:



Bonus point assignment - week 2

Create a java program that accepts user input and presents a menu with options.


- 1. Is number odd?
- 2. Is number a power of 2?
- 3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Paste source code here, with a screenshot of a working application.


1)

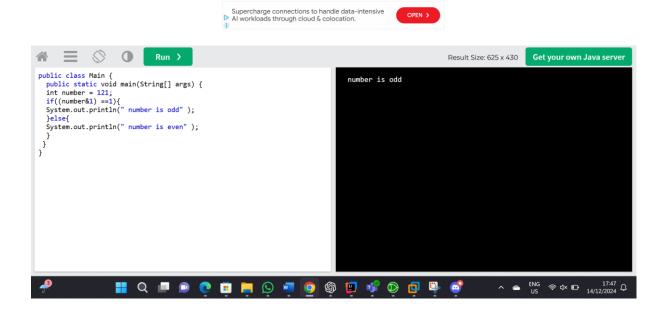

2)

```
public class Main {
    public static void main(String[] args) {
        int number = 4;
        if((number e (number - 1)) == 0 && number > 0) {
            System.out.println(" power of two" );
        } else{
            System.out.println(" not power of two" );
        }
    }
}
```

3)

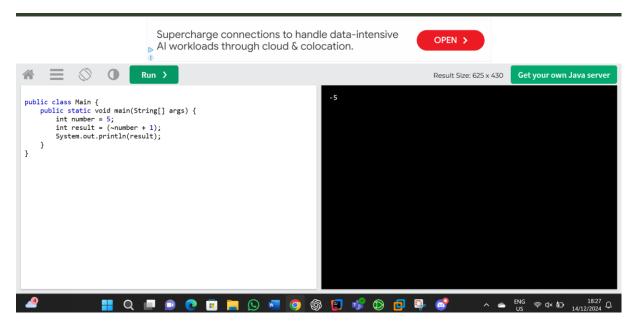

Ready? Then save this file and export it as a pdf file with the name: week2.pdf